

EXP 3 – SHIFT RESISTER

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.

--library UNISIM;


--use UNISIM.VComponents.all;

entity shiftreg is
    Port (
        si : in  STD_LOGIC;
        clk : in  STD_LOGIC;
        so : out  STD_LOGIC;
        pin : in  STD_LOGIC_VECTOR (3 downto 0);
        po : out  STD_LOGIC_VECTOR (3 downto 0);
        sel : in  STD_LOGIC_VECTOR (1 downto 0));
end shiftreg;

architecture Behavioral of shiftreg is
    signal temp:STD_LOGIC_VECTOR( 3 downto 0);

    begin
        process(clk)
        begin
            if(clk'event and clk='1')then
                case sel is
                    when "00"=> temp<= si&temp(3 downto 1);
```
 
```
so <=temp(3);  
  
when"01"=> temp<= si&temp(3 downto 1);  
  
po<=temp;  
  
when others=>null;  
  
end case;  
  
end if;  
  
end process;  
  
end Behavioral;
```



TEST BENCH

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY shifttest IS

END shifttest;

ARCHITECTURE behavior OF shifttest IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT shiftreg

    PORT(

        si : IN    std_logic;

        clk : IN    std_logic;

        so : OUT    std_logic;

        pin : IN    std_logic_vector(3 downto 0);

        po : OUT    std_logic_vector(3 downto 0);

        sel : IN    std_logic_vector(1 downto 0)

    );

    END COMPONENT;

    --Inputs

    signal si : std_logic := '0';

    signal clk : std_logic := '0';

    signal pin : std_logic_vector(3 downto 0) := (others => '0');

    signal sel : std_logic_vector(1 downto 0) := (others => '0');

    --Outputs

    signal so : std_logic;

    signal po : std_logic_vector(3 downto 0);
```

```

-- Clock period definitions

constant clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)

    uut: shiftreg PORT MAP (

        si => si,

        clk => clk,

        so => so,

        pin => pin,

        po => po,

        sel => sel

    );

    -- Clock process definitions

    clk_process :process

    begin

        clk <= '0';

        wait for clk_period/2;

        clk <= '1';

        wait for clk_period/2;

    end process;

    -- Stimulus process

    stim_proc: process

    begin

        sel<="00";

        si<='1';

        -- hold reset state for 100 ns.

        wait for 100 ns;

        sel<="01";

        si<='1';

```

```

wait for 100 ns;

sel<="10";

pin<="1100";

wait for 100 ns;

sel<="11";

pin<="1100";

--wait for clk_period*10;


-- insert stimulus here

wait;

end process;

END;

```

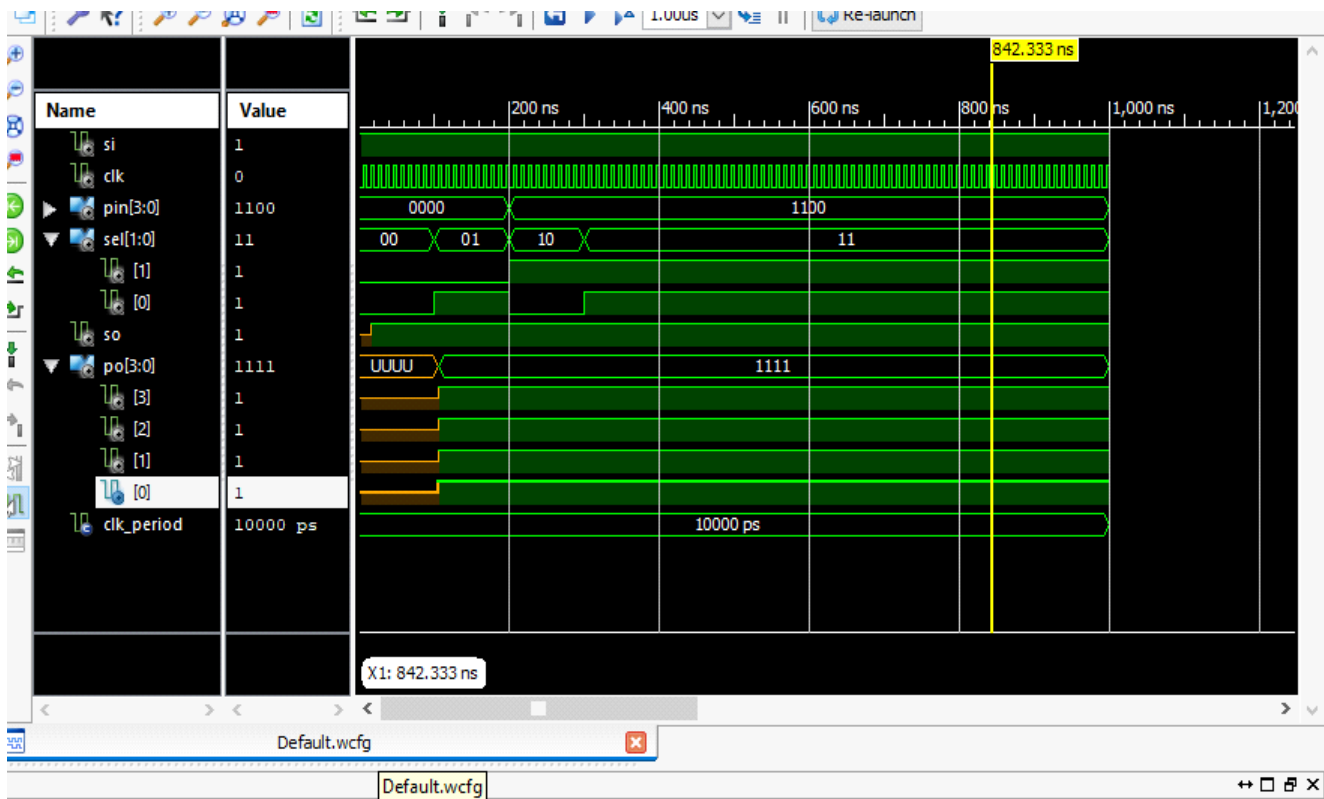

UCF FILE (SHIFT REGISTER)

NET clk LOC = P183;
NET Reset LOC = P102;
NET md(0) LOC = P101;
NET md(1) LOC = P100;
NET si LOC = P97;
NET so LOC = P156;
NET pi(0) LOC = P87;
NET pi(1) LOC = P86;
NET pi(2) LOC = P85;
NET pi(3) LOC = P81;
NET po(0) LOC = P162;
NET po(1) LOC = P165;
NET po(2) LOC = P166;
NET po(3) LOC = P167;

Final Report

Final Results

RTL Top Level Output File Name : shiftreg.ngc
Top Level Output File Name : shiftreg
Output Format : NGC
Optimization Goal : Speed
Keep Hierarchy : No

Design Statistics

IOs : 13
Cell Usage :
BELS : 6
LUT2 : 2
LUT3 : 4

# FlipFlops/Latches	: 9
# FD	: 4
# FDE	: 5
# Clock Buffers	: 1
# BUFGP	: 1
# IO Buffers	: 8
# IBUF	: 3
# OBUF	: 5

=====

Device utilization summary:

Selected Device : 3s400pq208-5

Number of Slices:	5	out of	3584	0%
Number of Slice Flip Flops:	9	out of	7168	0%
Number of 4 input LUTs:	6	out of	7168	0%
Number of IOs:	13			
Number of bonded IOBs:	9	out of	141	6%
Number of GCLKs:	1	out of	8	12%

Partition Resource Summary:

No Partitions were found in this design.

TIMING REPORT

NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE.

FOR ACCURATE TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT
GENERATED AFTER PLACE-and-ROUTE.

Clock Information:

-----+-----+-----+

Clock Signal		Clock buffer(FF name)		Load	
--------------	--	-----------------------	--	------	--

-----+-----+-----+
clk

| BUFGP

| 9

|

-----+-----+-----+
Asynchronous Control Signals Information:

No asynchronous control signals found in this design

Timing Summary:

Speed Grade: -5

Minimum period: 2.230ns (Maximum Frequency: 448.340MHz)

Minimum input arrival time before clock: 3.538ns

Maximum output required time after clock: 6.216ns

Maximum combinational path delay: No path found

Timing Detail:

All values displayed in nanoseconds (ns)

EXP 4 – MOD –N COUNTER

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_unsigned.ALL;

use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity mod5ex is
    Port ( clk : in  STD_LOGIC;
          clr : in  STD_LOGIC;
          q : inout STD_LOGIC_VECTOR (2 downto 0));
end mod5ex;

architecture Behavioral of mod5ex is
    signal count: std_logic_vector(2 downto 0);

begin
    process(clk)
    begin
        if (clr='1') then count <= "000";

        elsif (rising_edge (clk)) then

            if (count="100")
            then count <= "000";

            else
```

```
count<=count+ 1;
```


```
end if;
```

```
end if;
```

```
end process;
```

```
q<=count;
```

```
end Behavioral;
```

 

TEST BENCH

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY mod5test IS

END mod5test;

ARCHITECTURE behavior OF mod5test IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT mod5ex

    PORT(

        clk : IN    std_logic;

        clr : IN    std_logic;

        q : INOUT   std_logic_vector(2 downto 0)

    );

    END COMPONENT;

    --Inputs

    signal clk : std_logic := '0';

    signal clr : std_logic := '0';

    --BiDirs

    signal q : std_logic_vector(2 downto 0);

    -- Clock period definitions

    constant clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)

    uut: mod5ex PORT MAP (
```

```

        clk => clk,

        clr => clr,

        q => q

    );

-- Clock process definitions

clk_process :process

begin

    clk <= '0';

    wait for 10 ns;

    clk <= '1';

    wait for 10 ns;

end process;

-- Stimulus process

stim_proc: process

begin

    clr<='1';

    -- hold reset state for 100 ns.

    wait for 20 ns;

    clr<='0';

    -- hold reset state for 100 ns.

    wait for 20 ns;

    -- hold reset state for 100 ns.

--    wait for 100 ns;

--    wait for clk_period*10


    -- insert stimulus here

    wait;

end process;

```

END;

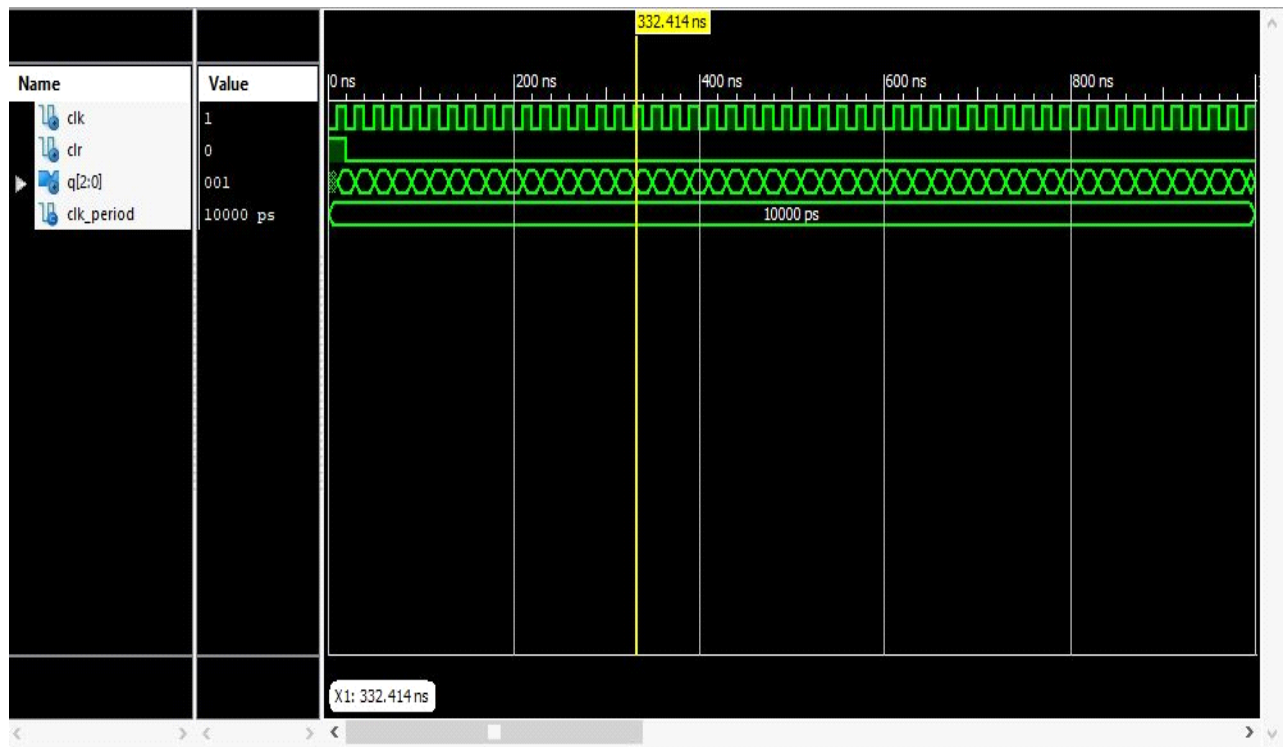

Final Report

```
=====
*                               Final Report                               *
=====
```

Final Results

RTL Top Level Output File Name : mod5ex.ngr

Top Level Output File Name : mod5ex

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : No

Design Statistics

IOs : 5

Cell Usage :

# BELS	: 3
# LUT2	: 1
# LUT3	: 2
# FlipFlops/Latches	: 3
# FDC	: 3
# Clock Buffers	: 1
# BUFGP	: 1
# IO Buffers	: 4
# IBUF	: 1
# OBUF	: 3

=====

Device utilization summary:

Selected Device : 3s400pq208-5

Number of Slices:	2	out of	3584	0%
Number of Slice Flip Flops:	3	out of	7168	0%
Number of 4 input LUTs:	3	out of	7168	0%
Number of IOs:	5			
Number of bonded IOBs:	5	out of	141	3%
Number of GCLKs:	1	out of	8	12%

Partition Resource Summary:

No Partitions were found in this design.

EXP 5 – FIFO

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

use IEEE.numeric_std.all;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.

--library UNISIM;

--use UNISIM.VComponents.all;

entity fifo_vhdl is
    Port ( clk,rst : in STD_LOGIC;

           enr : in STD_LOGIC;      --enable read,should be '0' when not in use.
           enw : in STD_LOGIC;      --enable write,should be '0' when not in use.
           dataout : out STD_LOGIC_VECTOR (3 downto 0);    --output data
           datain : in STD_LOGIC_VECTOR (3 downto 0);      --input data
           FF_empty,clk_div : out STD_LOGIC;    --set as '1' when the queue is empty
           FF_full : out STD_LOGIC);    ---set as '1' when the queue is full
end fifo_vhdl;

architecture Behavioral of fifo_vhdl is

type memory_type is array (0 to 7) of std_logic_vector(3 downto 0);

signal memory: memory_type :=(others=>(others=> '0'));

signal readptr,writeptr: std_logic_vector(2 downto 0) := "000";

signal count : std_logic_vector(2 downto 0):="000";
```

```

signal newclk : std_logic;

signal count1 : std_logic_vector(25 downto 0);

begin
-----

clk_div1: process(clk,rst)
begin
if rst='1' then
count1<=(others =>'0');
elsif clk'event and clk='1' then
count1<=count1+'1';
end if;
end process;
-----

newclk<=count1(25);
clk_div<=count1(25);
-----

fifo_empty_full: process(readptr,writeptr,count)
begin
if(count="000") then
FF_empty<='1';
FF_full<='0';
elsif(count="111")then
FF_empty<='0';
FF_full<='1';
end if;
end process;
-----

count1_reptr_wdptr: process(newclk,rst,enr,enw,readptr,writeptr)

```



```

begin
if rst='1' then
count<="000";
readptr<=(others=>'0');
writeptr<=(others=>'0');

    else if newclk'event and newclk='1' then
        if enw='1' and enr='0' then
            count<=count+'1';

            if count="111" then
                count<=count;
            end if;

            readptr<=readptr;
            writeptr<=writeptr+1;

            elsif enw='0' and enr='1' then
                count<=count-'1';

                if count="000" then
                    count<=count;
                end if;

                readptr<=readptr+1;
                writeptr<=writeptr;
            end if;
        end if;
    end if;

end process;

-----

mem_read_write:process(newclk,count,enw,enr)

```

```

begin

if(newclk'event and newclk='1') then

if enw='1' and enr='0' then

if count /="111" then

memory(conv_integer(writeptr))<=datain;

end if;

elsif enr='0' and enw='1' then

if count /="000" then

dataout<=memory(conv_integer(readptr));

end if;


end if;

end if;

end process;

end Behavioral;

```

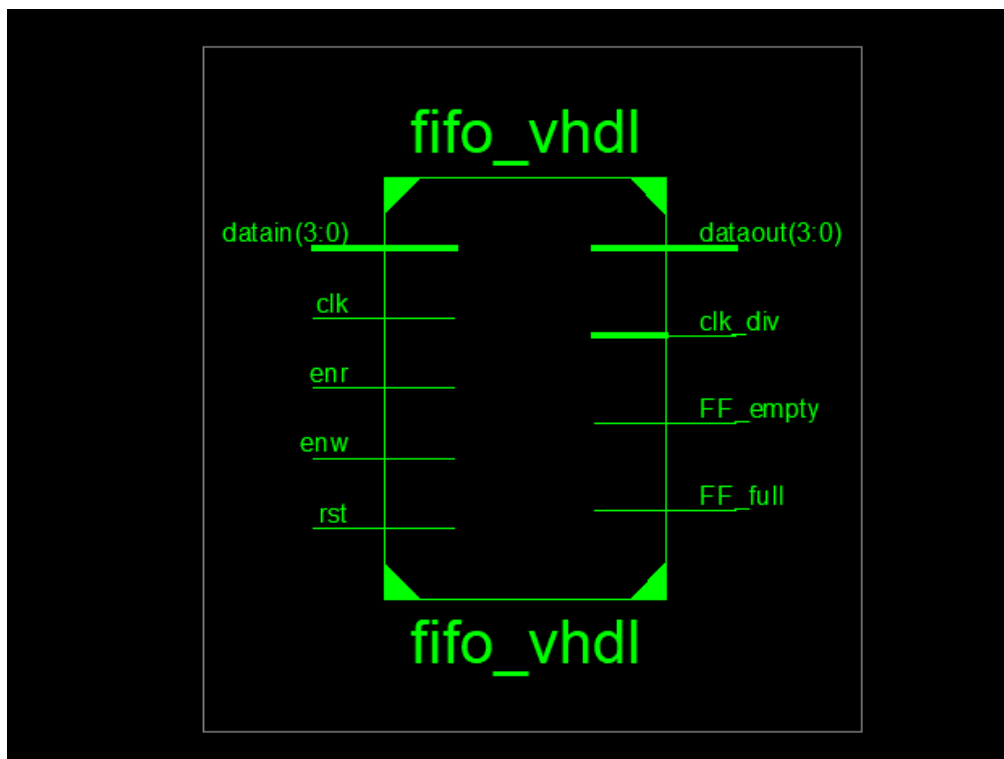

TEST BENCH

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY fifo_test IS

END fifo_test;

ARCHITECTURE behavior OF fifo_test IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT fifo_vhdl

    PORT(

        clk : IN    std_logic;

        rst : IN    std_logic;

        enr : IN    std_logic;

        enw : IN    std_logic;

        dataout : OUT std_logic_vector(3 downto 0);

        datain : IN  std_logic_vector(3 downto 0);

        FF_empty : OUT std_logic;

        clk_div : OUT  std_logic;

        FF_full : OUT  std_logic

    );

END COMPONENT;
```

--Inputs

signal clk : std_logic := '0';

signal rst : std_logic := '0';

signal enr : std_logic := '0';

signal enw : std_logic := '0';

signal datain : std_logic_vector(3 downto 0) := (others => '0');

--Outputs

signal dataout : std_logic_vector(3 downto 0);

signal FF_empty : std_logic;

signal clk_div : std_logic;

signal FF_full : std_logic;

-- Clock period definitions

constant clk_period : time := 10 ns;

constant clk_div_period : time := 10 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: fifo_vhdl PORT MAP (

clk => clk,

rst => rst,

enr => enr,

enw => enw,

dataout => dataout,

datain => datain,

FF_empty => FF_empty,

```

        clk_div => clk_div,

        FF_full => FF_full

    );

-- Clock process definitions

clk_process :process
begin

    clk <= '0';

    wait for clk_period/2;

    clk <= '1';

    wait for clk_period/2;

end process;


clk_div_process :process
begin

    clk_div <= '0';

    wait for clk_div_period/2;

    clk_div <= '1';

    wait for clk_div_period/2;

end process;

-- Stimulus process

stim_proc: process
begin

    -- hold reset state for 100 ns.

    rst<='1';

    enr<='0';

    enw<='1';

    dataout<="0110";

```

```

wait for 100 ns;

rst<='0';

enr<='0';

enw<='1';

dataout<="1100";

wait for 100 ns;

rst<='0';

enr<='1';

enw<='0';

dataout<="1100";

wait for 100 ns;

wait for clk_period*10;


-- insert stimulus here

wait;

end process;

END;

```

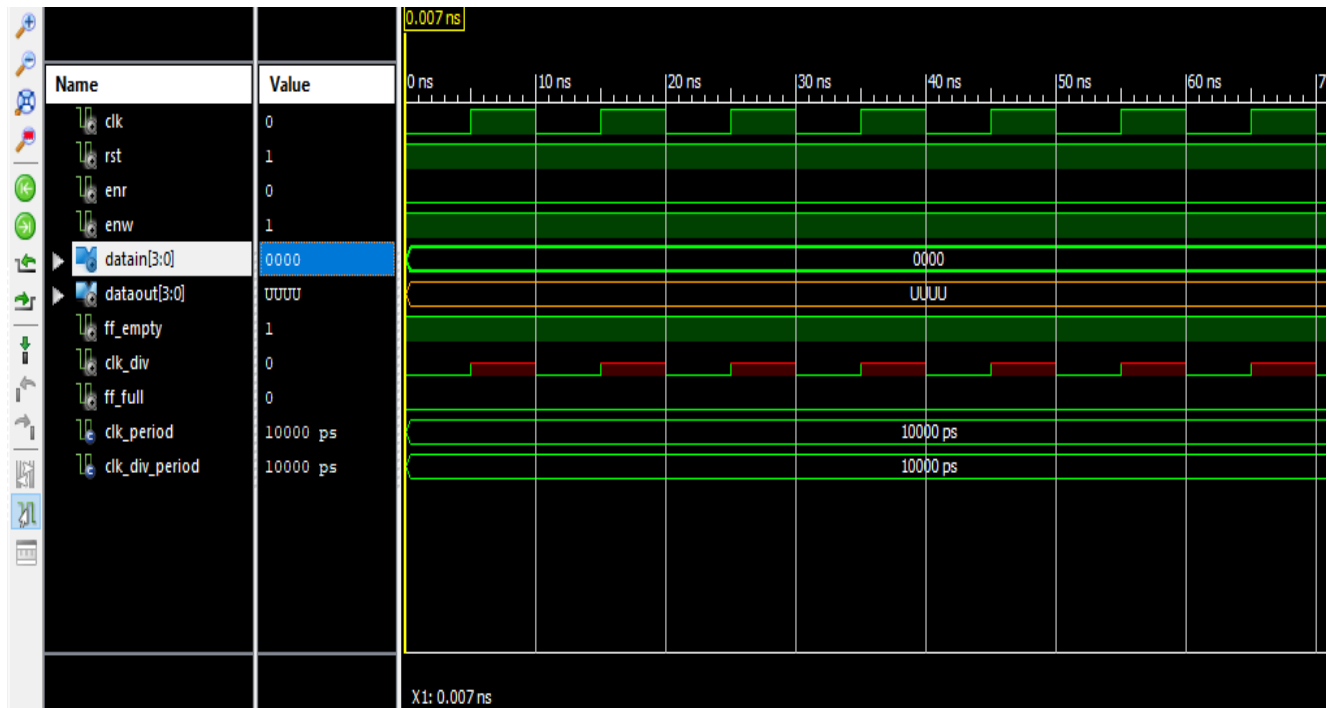

=====

* Final Report *

=====

Final Results

RTL Top Level Output File Name : fifo_vhdl.ngr

Top Level Output File Name : fifo_vhdl

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : No

Design Statistics

IOs : 15

Cell Usage :

BELS : 96

GND : 1

INV : 4

LUT1 : 25

LUT2 : 4

LUT3 : 6

LUT4 : 4

MUXCY : 25

VCC : 1

XORCY : 26

FlipFlops/Latches : 41

FDC : 26

FDCE : 9

```

#      FDE                      : 4
#      LD                      : 2
# RAMS                      : 4
#      RAM16X1D                : 4
# Clock Buffers              : 1
#      BUFGP                    : 1
# IO Buffers                  : 14
#      IBUF                      : 7
#      OBUF                      : 7

```

```
=====
```

Device utilization summary:

```
-----
```

Selected Device : 3s400pq208-5

Number of Slices:	25	out of	3584	0%
Number of Slice Flip Flops:	39	out of	7168	0%
Number of 4 input LUTs:	51	out of	7168	0%
Number used as logic:	43			
Number used as RAMs:	8			
Number of IOs:	15			
Number of bonded IOBs:	15	out of	141	10%
IOB Flip Flops:	2			
Number of GCLKs:	1	out of	8	12%

```
-----
```

Partition Resource Summary:

```
-----
```

No Partitions were found in this design.

EXP 6 – LCD

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity LCD_SIMPLE_Practice is
    Port ( rst,clk : in  STD_LOGIC;
          lcd_RS : out  STD_LOGIC;
          -- din : in std_logic_vector(7 downto 0);
          --LED : OUT std_logic_vector(7 downto 0);
          lcd_EN : out  STD_LOGIC;
          data_out : out  STD_LOGIC_VECTOR (7 downto 0));
    end LCD_SIMPLE_Practice;

architecture Behavioral of LCD_SIMPLE_Practice is
    signal div_count : std_logic_vector(20 downto 0);
    signal clk_new : std_logic;

    -----

    type state is(reset,fuction,mode,cur,clear,d0,d1,d2,fuction1,mode1,cur1,clear1,d01,d11,d21);

    signal pss,nx : state;

    begin

    --LED<=din;

    -----

    clk_DIV: process(clk,rst)
```

```

begin
if rst= '1' then

div_count<= (others=>'0');

elsif clk'event and clk='1' then

div_count<= div_count + '1';

end process;

```

```

-----

clk_new<= div_count(20);

-----

```

```

p_state_transactin: process (clk_new,rst)

begin

if rst='1' then

pss<=reset;

elsif clk_new'event and clk_new= '1' then

pss<= nx;

end if;

end process;

```

```

-----

LCD_working: process(pss)

begin

case pss is

when reset =>

lcd_RS<='0';

lcd_EN<='1';

nx<= fuction;

data_out<="00111100";  --3Ch

```

when fuction =>

lcd_RS<='0';

lcd_EN<='1';

data_out<="00111100"; --3Ch

nx<= fuction

when fuction1 =>

lcd_RS<='0';

lcd_EN<='0';

data_out<="00111100"; --3Ch

nx<= mode;

when mode =>

lcd_RS<='0';

lcd_EN<='1';

data_out<="00000110"; --06h

nx<= mode1;

when mode1 =>

lcd_RS<='0';

lcd_EN<='0';

data_out<="00000110"; --06h

nx<= cur;

when cur =>

lcd_RS<='0';

lcd_EN<='1';

data_out<="00001100"; --0Ch

```
nx<= cur1;
```

```
when cur1 =>
```

```
lcd_RS<='0';
```

```
lcd_EN<='0';
```

```
data_out<="00001100";    --0Ch
```

```
nx<= clear;
```

```
when clear =>
```

```
lcd_RS<='0';
```

```
lcd_EN<='1';
```

```
data_out<="00000001";    --01h
```

```
nx<= clear1;
```

```
when clear1 =>
```

```
lcd_RS<='0';
```

```
lcd_EN<='0';
```

```
data_out<="00000001";    --01h
```

```
nx<= d0;
```

```
when d0 =>
```

```
lcd_RS<='1';
```

```
lcd_EN<='1';
```

```
data_out<="01010011";    -----din;    --S
```

```
nx<= d01;
```

```
when d01 =>
```

```
lcd_RS<='1';  
lcd_EN<='0';  
data_out<="01010011";-----din;    --S  
nx<= d1;
```

```
when d1 =>  
  lcd_RS<='1';  
  lcd_EN<='1';  
  data_out<="01001011";    --K  
  nx<= d11;
```

```
when d11 =>  
  lcd_RS<='1';  
  lcd_EN<='0';  
  data_out<="01001011";    --K  
  nx<= d2;
```

```
when d2 =>  
  lcd_RS<='1';  
  lcd_EN<='1';  
  data_out<="01001110";    --N  
  nx<= d21;
```

```
when d21 =>  
  lcd_RS<='1';  
  lcd_EN<='0';  
  data_out<="01001110";    --N
```

```
nx<= d21;
```

```
when others=>
```


```
null;
```

```
end case;
```

```
end process;
```

```
end Behavioral;
```

LCD_SIMPLE_Practice

 

LCD_SIMPLE_Practice

TEST BENCH

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY LCDTEST IS

END LCDTEST;

ARCHITECTURE behavior OF LCDTEST IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT LCD_SIMPLE_Practice

    PORT(

        rst : IN  std_logic;

        clk : IN  std_logic;

        lcd_RS : OUT  std_logic;

        lcd_EN : OUT  std_logic;

        data_out : OUT  std_logic_vector(7 downto 0)

    );

    END COMPONENT;

--Inputs

signal rst : std_logic := '0';
signal clk : std_logic := '0';

--Outputs

signal lcd_RS : std_logic;
signal lcd_EN : std_logic;
signal data_out : std_logic_vector(7 downto 0);
```

```

-- Clock period definitions

constant clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)

    uut: LCD_SIMPLE_Practice PORT MAP (

        rst => rst,

        clk => clk,

        lcd_RS => lcd_RS,

        lcd_EN => lcd_EN,

        data_out => data_out

    );

    -- Clock process definitions

    clk_process :process
    begin

        clk <= '0';

        wait for clk_period/2;

        clk <= '1';

        wait for clk_period/2;

    end process;

    -- Stimulus process

    stim_proc: process
    begin

        rst<='1';

        -- hold reset state for 100 ns.

        wait for 100 ns;

rst<='0';

--din<="00101010";

        wait for 100 ns;

```



```

rst<='1';

--din<="00101010";

    -- hold reset state for 100 ns.

rst<='0';

--din<="00101010";

    wait for 100 ns;

rst<='1';

--din<="00111111";

--hold reset state for 100 ns.

    wait for 100 ns;

rst<='0';

    wait for 100 ns;

        -- insert stimulus here

        wait;

    end process;

END;

```



UCF FILE (LCD)

NET data(0) LOC = P62;

NET data(1) LOC = P63;

NET data(2) LOC = P64;

NET data(3) LOC = P65;

NET data(4) LOC = P67;

NET data(5) LOC = P68;

NET data(6) LOC = P71;

NET data(0) LOC = P72;

NET clk LOC = P183;

NET reset LOC = P102;

*

Final Report

*

=====

Final Results

RTL Top Level Output File Name : LCD_SIMPLE_Practice.ngc

Top Level Output File Name : LCD_SIMPLE_Practice

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : No

Design Statistics

IOs : 12

Cell Usage :

# BELS	: 83
# GND	: 1
# INV	: 1
# LUT1	: 20
# LUT2	: 2
# LUT3	: 5
# LUT4	: 11
# MUXCY	: 20
# MUXF5	: 1
# VCC	: 1
# XORCY	: 21
# FlipFlops/Latches	: 36
# FDC	: 34
# FDCE	: 1
# FDP	: 1
# Clock Buffers	: 1
# BUFGP	: 1
# IO Buffers	: 11
# IBUF	: 1
# OBUF	: 10

=====

=====

Device utilization summary:

Selected Device : 3s400pq208-5

Number of Slices: 23 out of 3584 0%

Number of Slice Flip Flops:	36	out of	7168	0%
Number of 4 input LUTs:	39	out of	7168	0%
Number of IOs:	12			
Number of bonded IOBs:	12	out of	141	8%
Number of GCLKs:	1	out of	8	12%

Partition Resource Summary:

No Partitions were found in this design.
